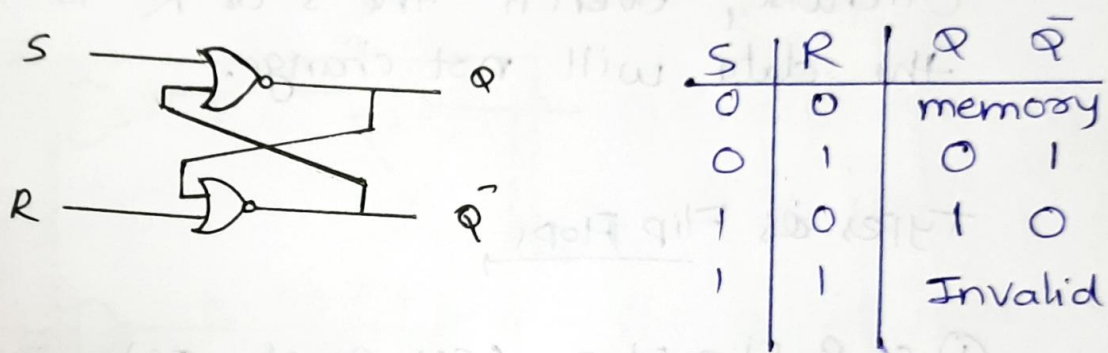


② Sequential logic circuits are digital circuits whose outputs depend not only on their current inputs but also on the past sequence of outputs.  
~~Inputs.~~

Example of sequential logic ckt,

SR Latch,



As shown above,

the output Q and  $\bar{Q}$  are given ~~with~~ as inputs of NOR gate with current input S and R. So, the output depends on current input as well as past outputs.

③

A flip-flop is a sequential digital electronic circuit having two stable states that can be used to store 1 bit of information. They are the fundamental building blocks of all memory devices.

The operation of Flip Flops depend on Input and clock. So, the output is changed only when you give an active clock signal.

Otherwise, even if the S or R is active the data will not change.


### Types of Flip Flops,

- ① S-R Flip Flop (Set-Reset FF).
- ② D Flip Flop (Data FF)
- ③ T Flip Flop (Toggle FF)
- ④ J-K Flip Flop



Race around

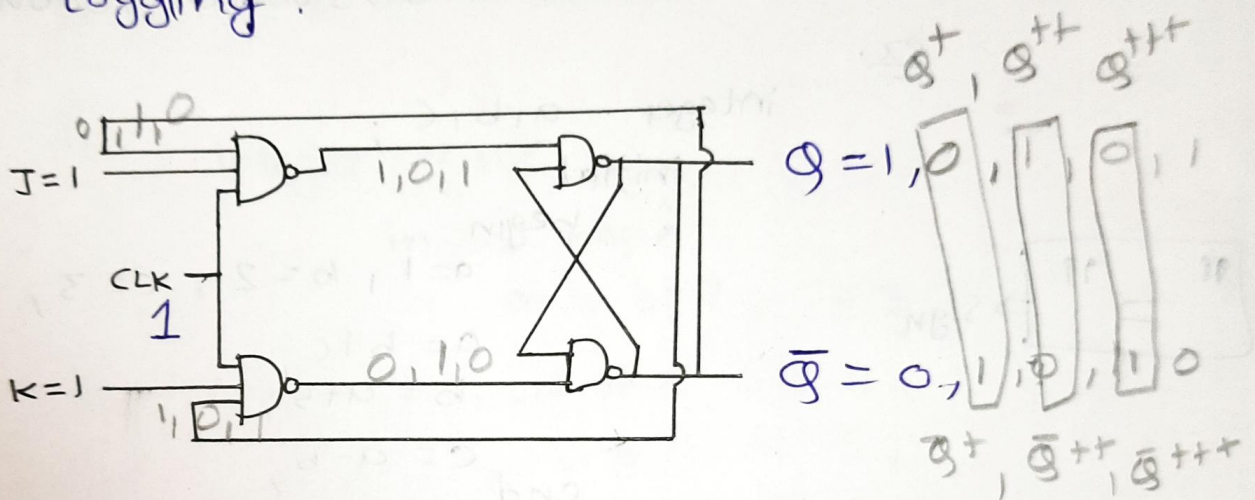In JK FF if  $J=K=1$  and  $CLK=1$  for long period or time, then Q output will toggle as long as CLK is High, which makes the output of the flip-flop is unstable. This is called race around in JK FF. In simple words Race around is Uncontrolled toggling.



assume  $Q=1$ ,

If we give  $J=K=1$ ,  $Q=0$ ,  $\bar{Q}=1$ ,

$Q$  &  $\bar{Q}$  are inputs to the nand gate

which makes output of first nand gate

to 0,1 which goes to the SR Latch,

which gives output as 1,0. similarly for

so, we are getting Q as

next interval.

$Q = 1, 0, 1, 0, 1, 0$

as long as CLK is high